

Reg. No. :

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

Question Paper Code : 20922

B.E./B.Tech. DEGREE EXAMINATIONS, NOVEMBER/DECEMBER 2023

Second Semester

Electronics and Communication Engineering

EC 3251 – CIRCUIT ANALYSIS

(Common to Electronics and Telecommunication Engineering)

(Regulations 2021)

Time : Three hours

Maximum : 100 marks

Answer ALL questions.

PART A — ($10 \times 2 = 20$ marks)

1. In a circuit consisting of two 50Ω resistors connected in series and third resistor R is connected across the series resistors. The equivalent resistance is found to be 60Ω . Calculate the resistance value, R .
2. Find the value of the current I , for the circuit shown in Fig. 1

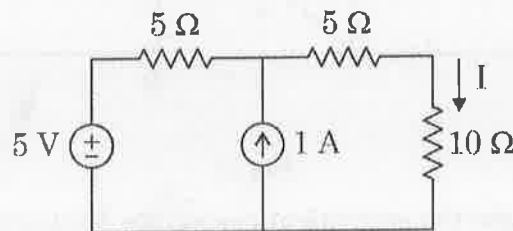


Fig. 1

3. Recall the statement of Norton's theorem.
4. Draw the dual of the network shown in Fig. 2

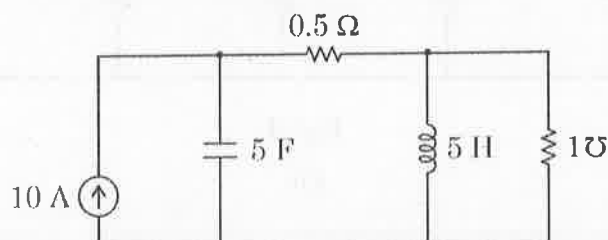


Fig. 2

5. Show the waveform representation of applied voltage across inductor, and the resulting current and the power.
6. A voltage of $240 \sin 377t$ is applied to a 6Ω resistor. Find the instantaneous power and average power.
7. Calculate the impedance at resonance for an RLC series circuit, having $R = 20\Omega$, $L = 50\text{ mH}$, and $C = 1\mu\text{F}$.
8. An RC series circuit has $R = 20\Omega$ and $C = 400\mu\text{F}$. What is its time constant?
9. Two 2H inductance coils are connected in series and are also magnetically coupled to each other, the coefficient of coupling being 0.1 . Find the total inductance of the combination.
10. List the properties of incidence matrix.

PART B — ($5 \times 13 = 65$ marks)

11. (a) (i) Determine the potential difference across A and B, V_{AB} in the circuit shown in Fig. 3. (9)

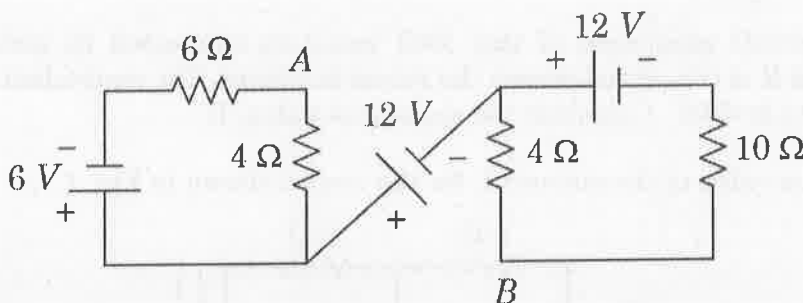


Fig. 3

- (ii) Calculate the equivalent resistance between the terminals A and B of circuit shown in Fig. 4. (4)

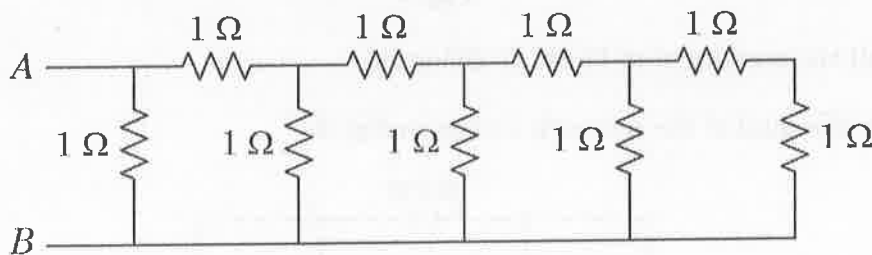


Fig. 4

Or

- (b) (i) Determine the voltage drop across all the resistances for the circuit shown in Fig. 5. using nodal analysis (6)

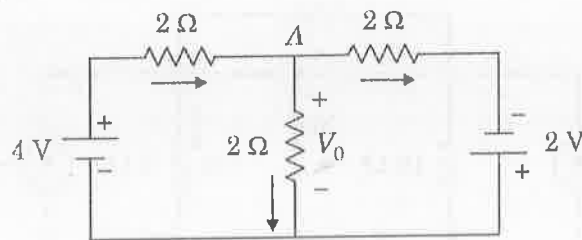


Fig. 5

- (ii) Determine the current passing through $15\ \Omega$ resistor in the circuit shown in Fig. 6 using mesh analysis. (7)

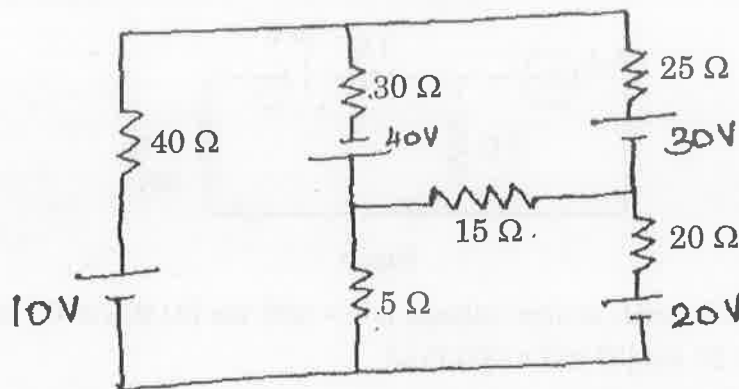


Fig. 6

12. (a) Determine the value of R_L for maximum power transfer in Fig. 7. Also find the maximum power.

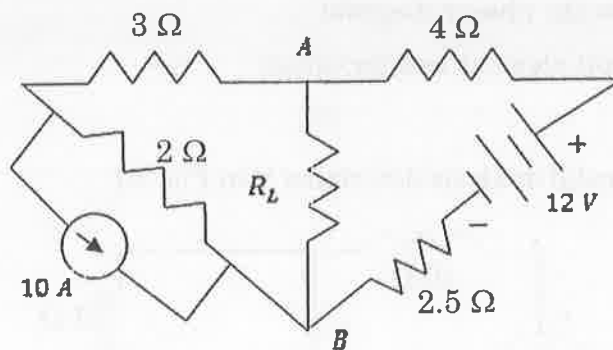


Fig. 7

Or

- (b) (i) Determine i_x for the following network shown in Fig. 8. (7)

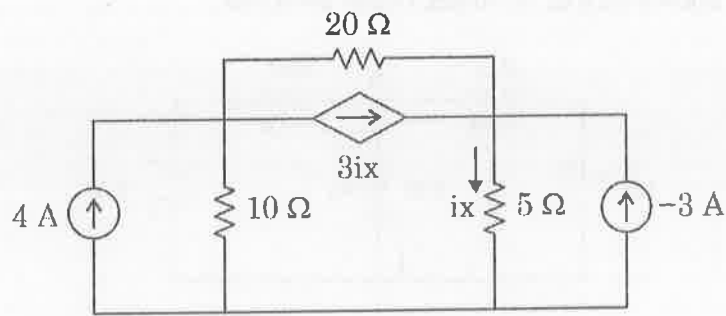


Fig. 8

- (ii) Using Thevenin's theorem, Calculate the power loss in R_L in Fig. 9. (6)

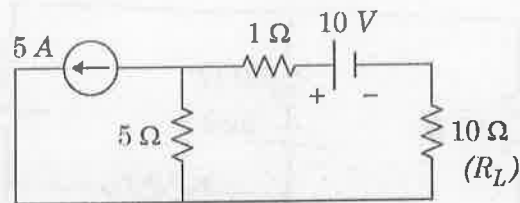


Fig. 9

13. (a) In the circuit, source voltage is $v = 200 \sin [314t + (\pi/6)]$ and the current is $i = 20 \sin.[314t - (\pi/3)]$ Find
- frequency
 - Maximum values of voltage and current
 - RMS value of voltage and current
 - Average values of both
 - Draw the phasor diagram
 - Circuit element and its values

Or

- (b) (i) By nodal analysis determine V in Fig. 10. (6)

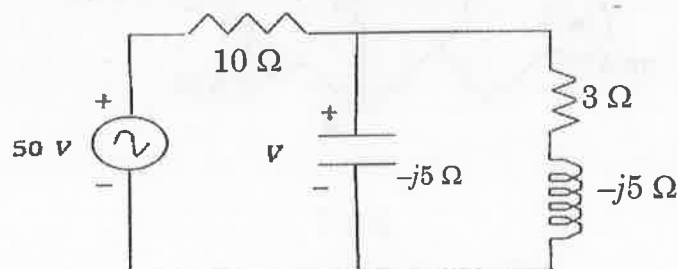


Fig. 10

- (ii) For the network shown in Fig. 11, Calculate the voltage across $7\ \Omega$ using Nortons theorem. (7)

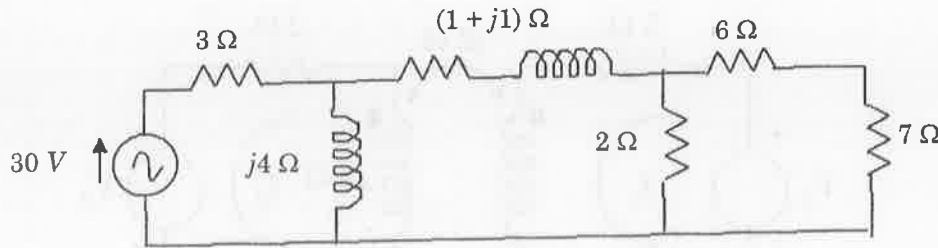


Fig. 11

14. (a) (i) Show that $\omega_1 \omega_2 = \omega_r^2$ for a series resonant circuit. (6)
- (ii) A coil has a resistance of $20\ \Omega$ and inductance of $80\ \text{mH}$ and is connected in series with a $100\ \mu\text{F}$ capacitor across $200\ \text{V}$, $50\ \text{Hz}$ supply, Determine the resonant frequency. Also determine, at resonance, the circuit impedance and BW. (7)

Or

- (b) (i) Examine the transient response of RC series circuit for unit step input. (6)
- (ii) In the circuit of Fig. 12, the switch S has been in position 1 for sufficient time to establish steady-state conditions. The switch is then moved to position 2. Determine the current transient.

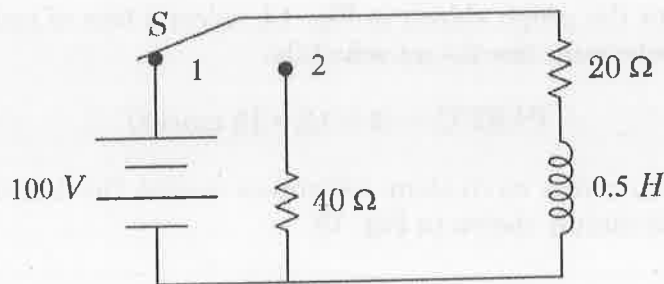


Fig. 12

15. (a) (i) Two identical coupled coils have an equivalent inductance of $80\ \text{mH}$ when connected series aiding, and $35\ \text{mH}$ series opposing. Calculate the self inductance of the coils, mutual inductance between them, and coefficient of coupling. (6)

- (ii) For the coupled circuit shown in Fig. 13, Show the ratio V_2/V_1 which results in zero current I_1 .

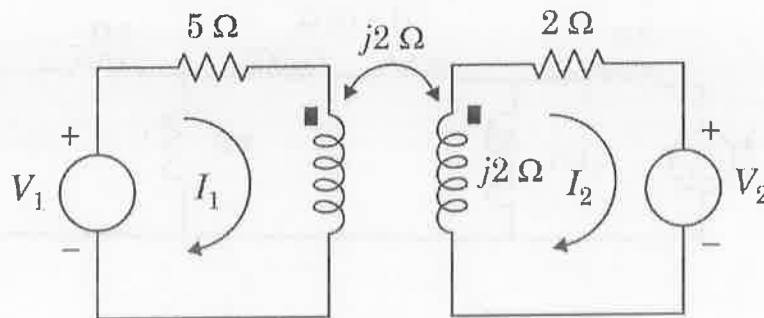


Fig. 13

Or

- (b) (i) The oriented graph of a network is shown in Fig. 14. Obtain the incidence matrix. (5)

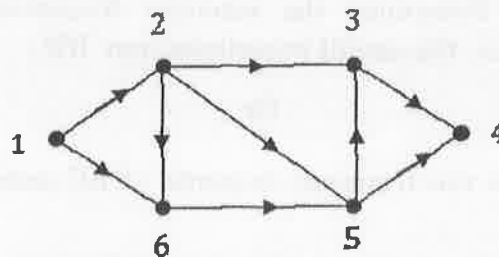


Fig. 14

- (ii) For the graph shown in Fig. 14, select a tree of your own choice and Determine the tie-set schedule. (8)

PART C — (1 × 15 = 15 marks)

16. (a) (i) Determine equivalent resistance across the terminals a and b for the circuit shown in Fig. 15. (8)

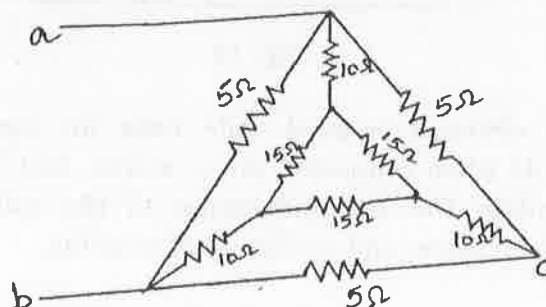


Fig. 15

- (ii) Find the voltage across the 2Ω resistor by using superposition theorem for the circuit shown in Fig. 16. (7)

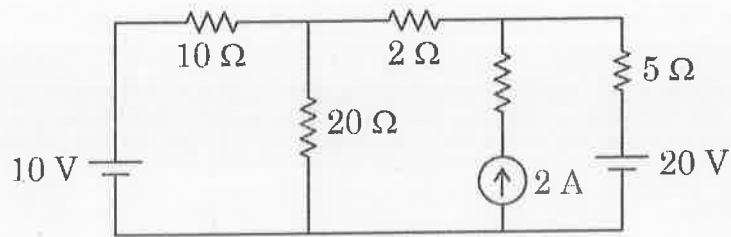


Fig. 16

Or

- (b) Analyze the transient response of RLC Series circuit for sinusoidal excitation.